

Solutions for Chapter 2

Exercise 2.1

We assume a forward voltage for the LED of 1.5V. Then for I_{LED} we have

$$I_{LED} = \frac{V_R}{R} = \frac{3.3V - 1.5V}{330\Omega} \approx \boxed{5.5mA}$$

To estimate the β_{min} we need the current entering the base

$$I_B = \frac{3.3V - 0.6V}{10k\Omega} = 0.27mA$$

Thus

$$\beta_{min} \geq \frac{I_{LED}}{I_B} = \boxed{20}$$

Exercise 2.2

NOTE: According to the errata 0.63 should be replaced by 0.76 and $63\mu\text{sec}$ by $76\mu\text{sec}$.

Starting from the hint that the capacitor charges from $-4.4V$ towards $+5V$, we would result to a total $9.4V$ for a full charge. However, the V_{BE} of Q_2 is clipping the charging process at only $5V$ of the total (from $-4.4V$ to $0.6V$). Thus, the capacitor will be 53% charged at the end.

Solving the voltage equation for a charging capacitor gives us

$$V_C(t) = V_f * (1 - e^{-\frac{t}{RC}})$$

set $V_C(t_1) = 0.53 * V_f$

$$0.53 = 1 - e^{-\frac{t_1}{R_3C_1}}$$

\Rightarrow

$$t_1 = -RC * \ln(0.47) \approx \boxed{0.76 * R_3C_1}$$